

Joseph Bofani, 12/10/2018, EET 223, Tachometer Project

Objectives-

- 1) Simulate the CD4026 (BCD to 7-segment counter IC) in VHDL
- 2) Transfer the VHDL program into a block file (.qsf)
- 3) Simulate a bicycle tachometer in a Quartus schematic using the block file
- 4) Build the same bicycle tachometer on a breadboard, with a switch (a press of the button simulates a rotation of the wheel)

VHDL Design-

Narrative:

- 1) The flow of logic is as follows: Counter → Decoder → 7-segment display
- 2) Required inputs on counter: *clear*, *count*, & *clock*
- 3) Required outputs on decoder: *carry out*, two *7-segment displays*
- 4) Program a counter in VHDL that has all required inputs
- 5) Program a BCD to 7-segment decoder in the same VHDL program
- 6) The output of the counter feeds into the input of the decoder
- 7) The decoder uses case statements to assign 7-segment integers to the 7-segment display
- 8) Test the validity of the counter using a waveform
 - a. The output should count from “0-9” and then reset to ‘0’
 - b. Carry-out goes HIGH only when ‘9’ is outputted HIGH from the

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5
6
7
8  entity TACHOMETERFINAL is
9
10 port( clock:   in std_logic;
11       clear:   in std_logic;
12       count:   in std_logic;
13       cout:    out std_logic;
14       bcd:     out std_logic_vector(6 downto 0));
15       --Q:      buffer std_logic_vector(3 downto 0));
16
17 end TACHOMETERFINAL;
18
19
20
21
22 architecture arc of TACHOMETERFINAL is
23     signal Pre_Q: std_logic_vector(3 downto 0);
24     signal Q: std_logic_vector(3 downto 0);
25     begin
26         -- behavior describe the counter
27     process(clock, count, clear)
28     begin
29
30         if clear='1' then
31             Pre_Q <= Pre_Q - Pre_Q;
32             cout <= '0';
33         elsif (clock='1' and clock'event) then
34             if count = '1' then
35                 Pre_Q <= Pre_Q + 1;
36                 cout <= '0';
37                 if Pre_Q = "1001" then
38                     Pre_Q <= Pre_Q - Pre_Q;
39                     end if;
40                 if Pre_Q = "1000" then
41                     cout <= '1';

```

METERFINAL_7_1200mv_85c_vhd_slow.sdo in folder "C:/intelFPGA_lite/TACHOMETER FINAL CODE/simulation/modelsim/" for EDA simulation tool
METERFINAL_7_1200mv_0c_vhd_slow.sdo in folder "C:/intelFPGA_lite/TACHOMETER FINAL CODE/simulation/modelsim/" for EDA simulation tool


```

31     Pre_Q <= Pre_Q - Pre_Q;
32     cout <= '0';
33     elsif (clock='1' and clock'event) then
34         if count = '1' then
35             Pre_Q <= Pre_Q + 1;
36             cout <= '0';
37             if Pre_Q = "1001" then
38                 Pre_Q <= Pre_Q - Pre_Q;
39                 end if;
40             if Pre_Q = "1000" then
41                 cout <= '1';
42                 end if;
43             end if;
44         end if;
45     Q <= Pre_Q; -- concurrent assignment statement
46     end process;
47
48 -- BEGIN DECODER
49
50
51 process (Q)
52 BEGIN
53
54 case Q is
55 when "0000" => bcd <= "0000001"; -- '0'
56 when "0001" => bcd <= "1001111"; -- '1'
57 when "0010" => bcd <= "0010010"; -- '2'
58 when "0011" => bcd <= "0000110"; -- '3'
59 when "0100" => bcd <= "1001100"; -- '4'
60 when "0101" => bcd <= "0100100"; -- '5'
61 when "0110" => bcd <= "0100000"; -- '6'
62 when "0111" => bcd <= "0001111"; -- '7'
63 when "1000" => bcd <= "0000000"; -- '8'
64 when "1001" => bcd <= "0000100"; -- '9'
65 when others => bcd <= "1111111"; -- BLANK
66
67 end case;
68 end process;
69 end arc;
70

```

METERFINAL_7_1200mv_85c_vhd_slow.sdo in folder "C:/intelFPGA_lite/TACHOMETER FINAL CODE/simulation/modelsim/" for EDA simulation tool
METERFINAL_7_1200mv_0c_vhd_slow.sdo in folder "C:/intelFPGA_lite/TACHOMETER FINAL CODE/simulation/modelsim/" for EDA simulation tool

VHDL design of the bicycle tachometer. Clock, count, and clear (reset) are all inputs in the counter, which is dictated by the first process (VHDL line 27 – 46). The counter is a positive-edge triggered device with an Active-HIGH clear. The counter resets when integer ‘9’ is reached (1001 in binary). The *cout* (carry-out) is activated when the counter reaches integer ‘8’ so the *cout* will only be read at the subsequent positive edge (integer ‘9’). The decoder begins at the second process (VHDL lines 51 – 68). The decoder uses the counter’s internal output, *Q*, as its input. Case statements are used to assign Active-LOW 7-segment display outputs (*bcd*) based on *Q*. If a number greater than 9 is counted, the 7-segment display will turn blank.

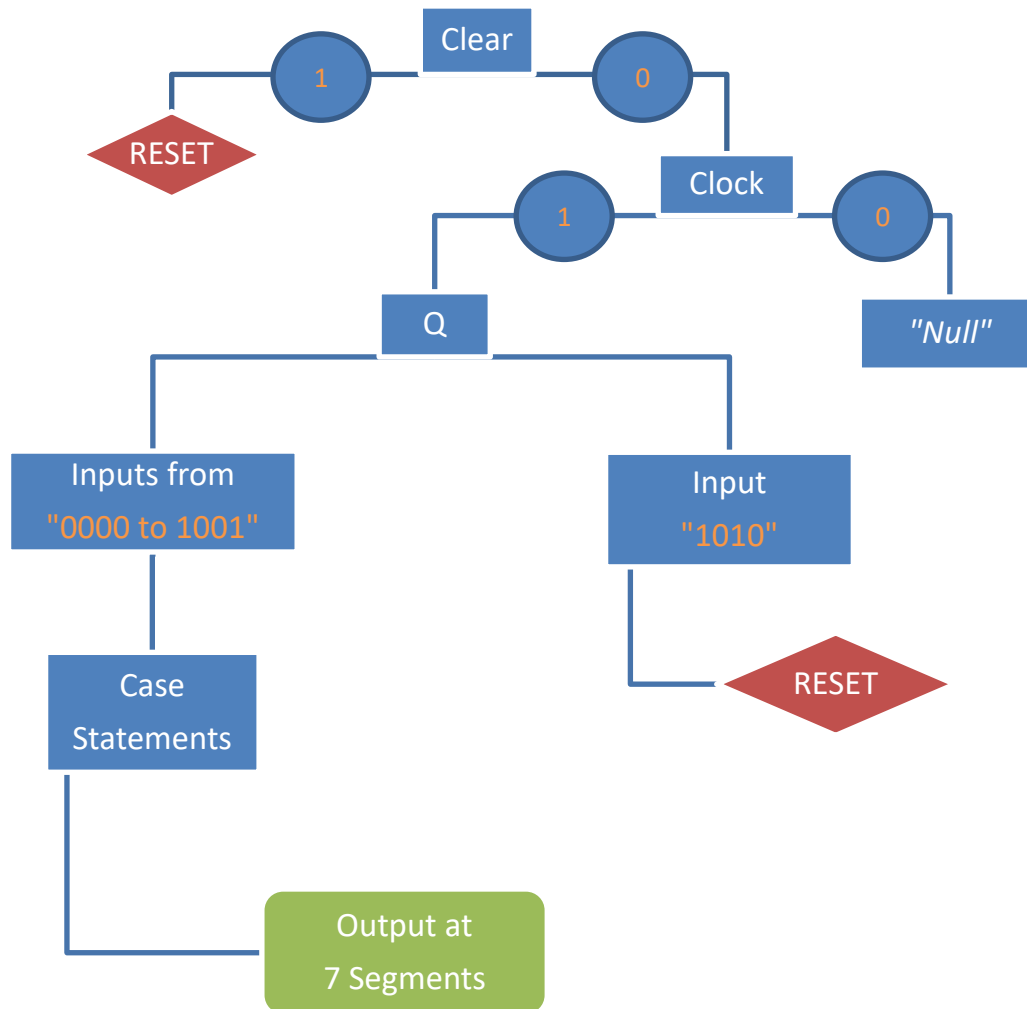

Logic hierarchy of the VHDL program. Orange text denotes a required input to continue down the current path. Orange '1' equals HIGH input, and an orange '0' equals LOW input.

```

library ieee ;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

```

```

-----

entity TACHOMETERFINAL is

```

```

    port(
        clock:    in std_logic;

        clear:    in std_logic;

        count:    in std_logic;

        cout:      out std_logic;

        bcd:      out std_logic_vector(6 downto 0));

        --Q:      buffer std_logic_vector(3 downto 0));

```

```

end TACHOMETERFINAL;

-----

```

```

architecture arc of TACHOMETERFINAL is

```

```

    signal Pre_Q: std_logic_vector(3 downto 0);

    signal Q: std_logic_vector(3 downto 0);

    begin

        -- behavior describe the counter

```

```

    process(clock, count, clear)

```

```

    begin

```

```

if clear= '1' then

    Pre_Q <= Pre_Q - Pre_Q;

    cout <= '0';

elsif (clock='1' and clock'event) then

    if count = '1' then

        Pre_Q <= Pre_Q + 1;

        cout <= '0';

        if Pre_Q = "1001" then

            Pre_Q <= Pre_Q - Pre_Q;

            end if;

        if Pre_Q = "1000" then

            cout <= '1';

            end if;

        end if;

    end if;

end if;

Q <= Pre_Q; -- concurrent assignment statement

end process;


-- BEGIN DECODER


process (Q)

BEGIN

case Q is

when "0000"=> bcd <="0000001"; -- '0'

when "0001"=> bcd <="1001111"; -- '1'

when "0010"=> bcd <="0010010"; -- '2'

when "0011"=> bcd <="0000110"; -- '3'

when "0100"=> bcd <="1001100"; -- '4'

```

```

when "0101"=> bcd <="0100100"; -- '5'

when "0110"=> bcd <="0100000"; -- '6'

when "0111"=> bcd <="0001111"; -- '7'

when "1000"=> bcd <="0000000"; -- '8'

when "1001"=> bcd <="0000100"; -- '9'


when others=> bcd <="1111111"; -- BLANK

```


```
end case;
```

```
end process;
```

```
end arc;
```

 

 Waveform of the VHDL program. The count resets after the integer '9' is reached. The *clear* is Active-HIGH at the start of the waveform. It is also observed that *cout* is only HIGH when '9' is counted. The *Q* is the internal count of the design, and isn't accounted for in the results of this waveform (only the *bcd* and *cout* outputs matter).




Zoomed in version of the VHDL program's waveform.


Quartus Schematic-

Narrative:

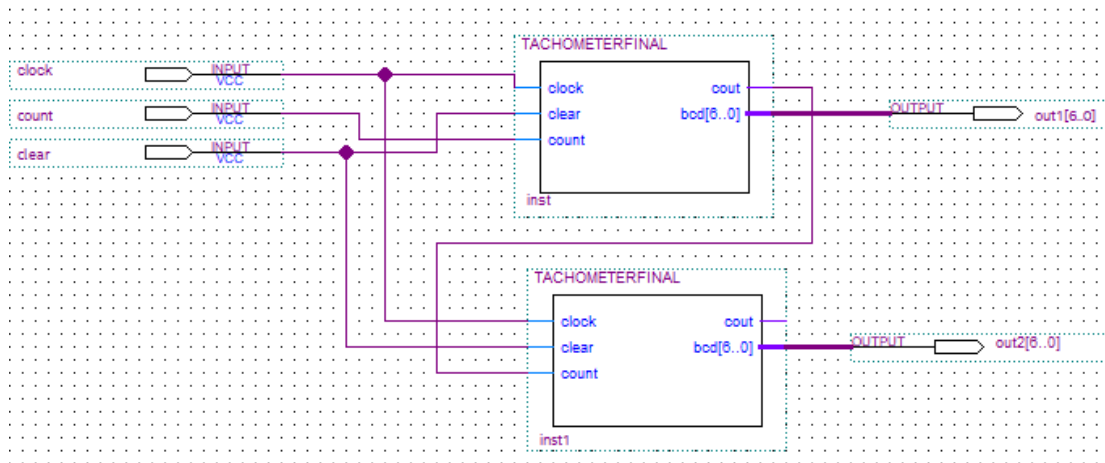
- 1) Convert VHDL into a .qsf block file
- 2) Build a bicycle tachometer by combining 2 newly created block files together in a schematic
- 3) Test the validity of the tachometer by using a waveform
 - a. The two outputs of the 7-segment displays should count from “0 – 99”



 Quartus schematic file that connects two custom-created chips that emulate the CD4026 ICs. Notice the *cout* of the first IC is the *count* of the second IC. The result is a tachometer that is hooked into two Active-LOW 7-segment displays, represented as *out1* and *out2*.



 Waveform for the schematic tachometer. *out1* represents the one's place, and *out2* represents the ten's place on the tachometer. The waveform can be observed to count from 0 – 35. *out1* takes 1 clock pulse to count up, whereas *out2* takes 10 clock pulses to count up.




Zoomed in version of the tachometer's (schematic) waveform.


Breadboard Circuit-

Narrative:

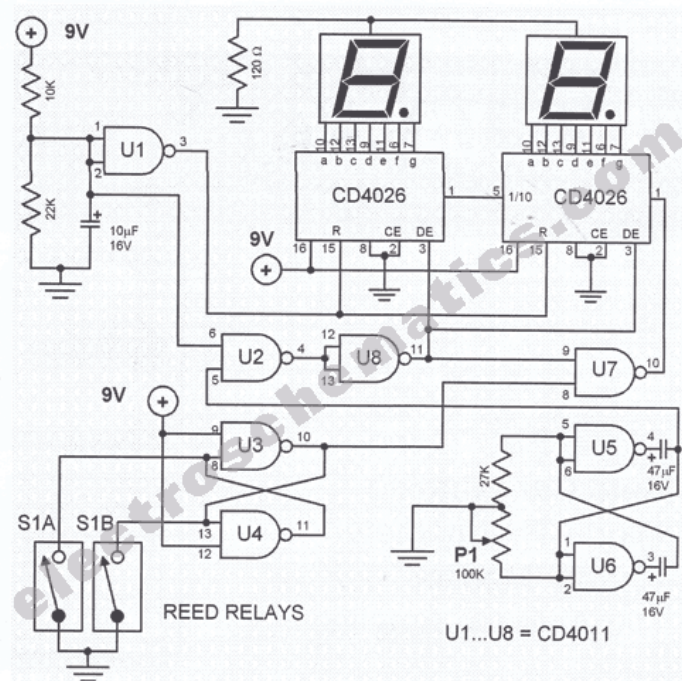
- 1) Build the tachometer circuit according to the below schematic
 - a. Test IC's and 7-segments to make sure they are functioning properly
 - b. 7-segments must be common cathode
 - c. Two CD4011 IC's are needed for the NAND gates
- 2) Attach power supply (9V and 500mA) and Ground to circuit
- 3) Test validity of tachometer
 - a. Circuit should display '0' at startup and consecutively count from "0-99" with each switch action
 - b. Circuit resets to '0' after "99" is displayed





Tachometer circuit schematic

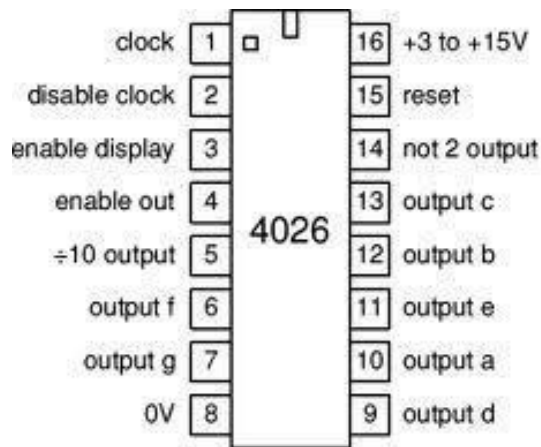


CD4026 7-segment decoder pinout

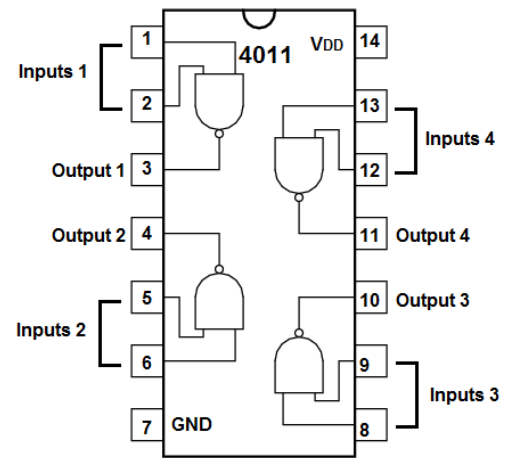

CD4011 NAND gate pinout

  

 Pinouts for two common types of 7-segments, which are both used in my circuit. Pinouts will vary between different types of 7-segments. For this project, the 7-segments must be common-cathode. Ground must be connected to where the above pinouts read “V_{CC}” or “Com.”



Fully functional tachometer circuit that's displaying "31." The '3' is in the ten's place, and the '1' is in the one's place. The circuit boots-up with a '0,' counts to "99," and then resets to '0'. The CD4011's are grouped adjacent on the top left, and the CD4026's are grouped adjacent to the left of the 7-segments.

Conclusion-

Coding the VHDL was best done in two programs; building the counter and decoder separately. Once they were both functioning, they could be programmed together with a common in and out line, which was Q in my code. The .bsf file and its respective VHDL file must be in the same computer folder in order for the block file to compile in a Quartus schematic. Before creating the physical circuit, it's crucial to test for broken parts. Pins on IC's can be broken, or components could be shorted from previous use. Two 7-segments I originally picked up had LED's that weren't working, so I had to swap out components. Also make sure that wires and pins do not overlap, and create an error in the logic. The logic of both the virtual and physical tachometer replicates each other. Both types of circuits have input flow through a counter, which passes data to a 7-segment decoder. From the decoders, the logic goes into two common-cathode (Active-LOW) 7-segment displays. Both types of circuits also reset to the startup value of '0' after the max number "99" is counted.